

## Chapter 5 Multiplexer and demultiplexer

### 5-1 Practice purpose

1. To understand digit multiplexer's theory and function
2. To understand digit demultiplexer's theory and function

### 5-2 Practice theory

A multiplexer (data selector)(MUX) connects input line to single output line and demultiplexer (data dispatcher)(DEMUX) is the opposite, which connects one input line to one of the many output lines. This chapter is mainly to discuss and practice these two electronic circuits.

#### 5-2-1

Multiplexer or data selector can choose many data inputs and only input one of them to output logic electronic circuit. The procedure to input data to the output end is controlled by select input. (Sometimes it is called address input). Figure 5-1 is the symbol of MUX. In this figure, the big arrow shows input and output with one or more lines.

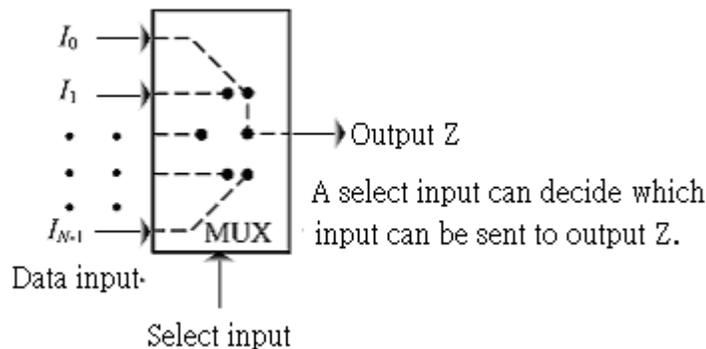


Figure 5-1 MUX symbols

The function of MUX is like a digital control multi positions switch \*. It means that select input's digit numbers can control the switch. The data input can be sent to output. For example, for certain selected inputs, input Z is like input  $I_0$ , but to other selected inputs, Z is like  $I_1$ , vice versa. In other words, MUX chooses one input from N inputs and sends it to the signal output and this is called multiplexing.

#### Basic two input multiplexers

Figure 5-2 shows data input  $I_0$  and  $I_1$  and select input S's two input MUX logic electronic circuit. We can decide which logic circuit to add to S input, which AND gate can be stimulated, and input data to output Z through OR gate. We can see the output formula is as:

$$Z = I_0 \bar{S} + I_1 S$$

$S = 0$ , so :


$$Z = I_0 \cdot 1 + I_1 \cdot 0$$

$$= I_0$$

It means that Z has the input signal  $I_0$ , and  $I_0$  can be a set logic circuit or spontaneous logic signal.  $S=1$ , so:

$$Z = I_0 \cdot 0 + I_1 \cdot 1 = I_1$$

It means z has input signal  $I_1$ .

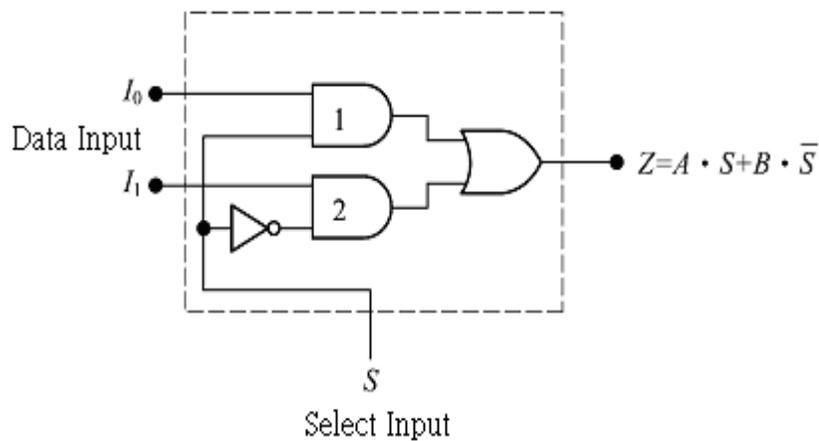

S	Input
0	$Z = I_0$
1	$Z = I_1$

Figure 5-2 Two MUX

### Four input MUX

As figure 5-3 shows, four input MUX is based on the same theory. It has four inputs and according to  $S_1, S_0$  select input four possible combinations to send four input choices to outputs. Each data input is combined with different select input circuit combination gate,  $I_0$  and  $S_1 S_0$ . When gates combine together, output  $I_0$  to Z through AND gate when  $S_1=0, S_0=0$ . The table shows the three input select codes' outputs.

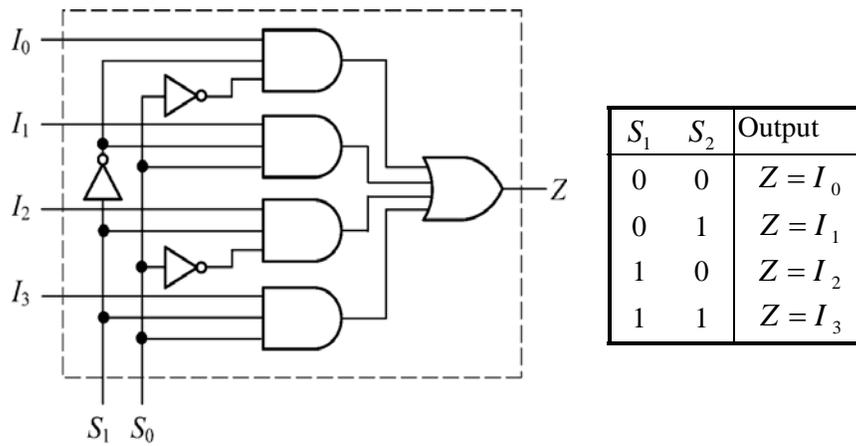


Figure 5-3 Four input MUX

### 5-2-2 De-multiplexer

Multiplexer can receive many inputs and send one to output. De-multiplexer, also called data dispatcher, only receives a single signal and dispatches to many outputs, which is opposite to multiplexer. Figure 5-4 is DEMUX figure, the big arrow represents one or many lines and the selected input code decides which data input goes to which outputs. In other words, DEMUX takes one input and dispatches it to N output through a multi position switch.


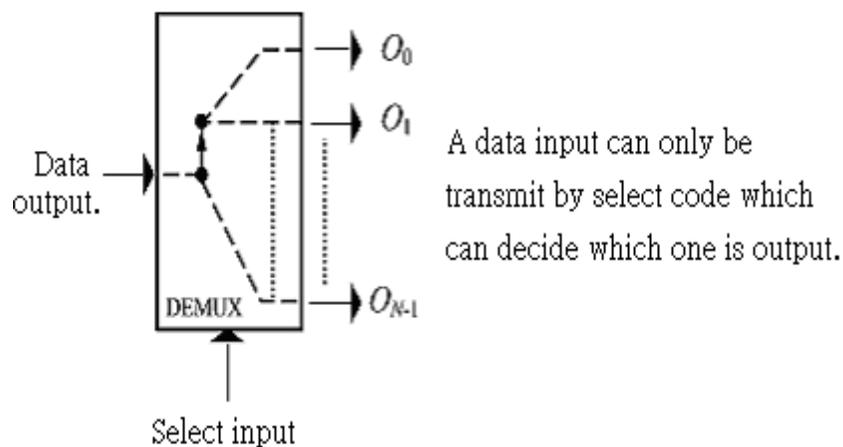


Figure 5-4 DEMUX

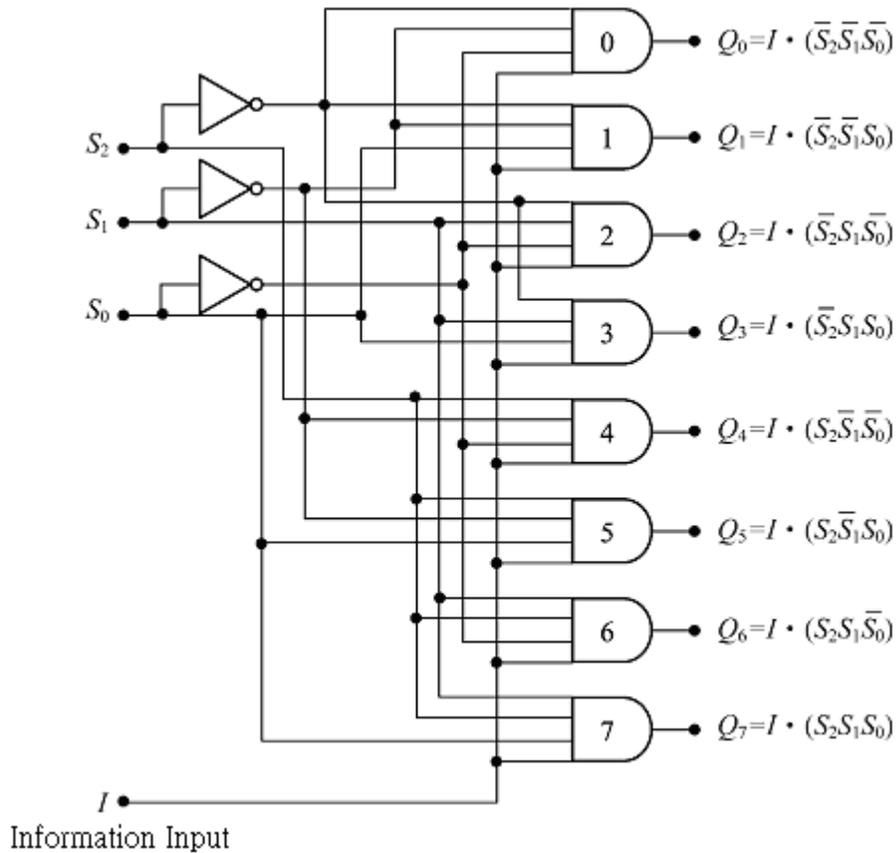

Select Code			Output							
$S_2$	$S_1$	$S_0$	$Q_7$	$Q_6$	$Q_5$	$Q_4$	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Figure 5-5 1 to 8 lines DEMUX

Figure 5-5 is 1-8 lines DEMUX. Single data input line I is connected to all eight AND gates, but only one of AND gates can be chosen. For example,  $S_2S_1S_0=000$ , only AND gate 0 is stimulated and the data input I is presented output  $Q_0$ . Its chosen code can send input I to other outputs. The truth table explains it.

## 5-3 Practice items

### 5-3-1

#### Experiment steps

1. 2 to 1 MUX circuit as figure 5-6

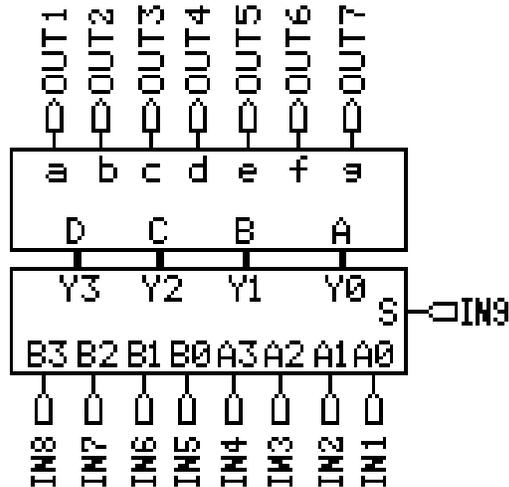


Figure 5-6

2. Input: Connect CON7 S1 to CON1 IN1  
Connect CON7 S2 to CON1 IN2  
Connect CON7 S3 to CON1 IN3  
Connect CON7 S4 to CON1 IN4  
Connect CON7 S5 to CON1 IN5  
Connect CON7 S6 to CON1 IN6  
Connect CON7 S7 to CON1 IN7  
Connect CON7 S8 to CON1 IN8  
Connect CON6 S9 to CON1 IN9  
Output: Connect CON4 OUT1 to 7- SEGMENT CON10 L1 a  
Connect CON4 OUT2 to 7-SEGMENT CON10 L1 b  
Connect CON4 OUT3 to 7- SEGMENT CON10 L1 c  
Connect CON4 OUT4 to 7-SEGMENT CON10 L1 d  
Connect CON4 OUT5 to 7- SEGMENT CON10 L1 e  
Connect CON4 OUT6 to 7-SEGMENT CON10 L1 f  
Connect CON4 OUT7 to 7- SEGMENT CON10 L1 g
3. Switch S1-S9 after finished connecting, as table 5-1. 0 means low logic, LED off.  
1 means high logic, LED on.
4. Record 7-segment changes in table 5-1.

S (S9)	A <sub>3</sub> (S4)	A <sub>2</sub> (S3)	A <sub>1</sub> (S2)	A <sub>0</sub> (S1)	B <sub>3</sub> (S8)	B <sub>2</sub> (S7)	B <sub>1</sub> (S6)	B <sub>0</sub> (S5)	Y <sub>3</sub> Y <sub>2</sub> Y <sub>1</sub> Y <sub>0</sub> Result
0	0	0	0	1	0	0	1	0	
0	0	0	1	1	0	1	0	0	
0	0	1	0	1	0	1	1	0	
1	0	0	0	1	0	0	1	0	
1	0	0	1	1	0	1	0	0	
1	0	1	0	1	0	1	1	0	

Table 5-1

5. From table 5-1, we know when  $S = 0$ ,  $Y = \underline{\hspace{1cm}}$ (A or B), when  $S = 1$ ,  $Y = \underline{\hspace{1cm}}$ (A or B).

5-3-2

Experiment steps

1. 4 to 1 MUX circuit as figure 5-7

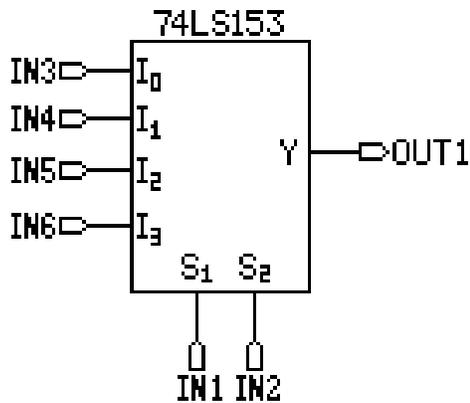


Figure 5-7

2. Input: Connect CON7 S1 to CON1 IN1  
 Connect CON7 S2 to CON1 IN2  
 Connect CON7 S3 to CON1 IN3  
 Connect CON7 S4 to CON1 IN4  
 Connect CON7 S5 to CON1 IN5  
 Connect CON7 S6 to CON1 IN6
- Output: Connect CON4 OUT1 to LED DISPLAY CON15 Q9
2. Switch S1-S6 after finished connecting, as table 5-2. 0 means low logic, LED off.  
 1 means high logic, LED on.
3. Record LED changes in table 5-2.

SOP	IN3 (S3)	IN4 (S4)	IN5 (S5)	IN6 (S6)	IN1 (S1)	IN2 (S2)	OUT1 (Q9)
0	0	0	0	0	0	0	
1	0	0	0	1	0	1	
2	0	0	1	0	1	0	
3	0	0	1	1	1	1	
4	0	1	0	0	0	0	
5	0	1	0	1	0	1	
6	0	1	1	0	1	0	
7	0	1	1	1	1	1	
8	1	0	0	0	0	0	
9	1	0	0	1	0	1	
10	1	0	1	0	1	0	
11	1	0	1	1	1	1	
12	1	1	0	0	0	0	
13	1	1	0	1	0	1	
14	1	1	1	0	1	0	
15	1	1	1	1	1	1	

Table 5-2

### 5-3-3 1 to 4 DMUX

#### Experiment steps

1. 1 to 4 DMUX circuit as figure 5-8 connecting the circuit properly.

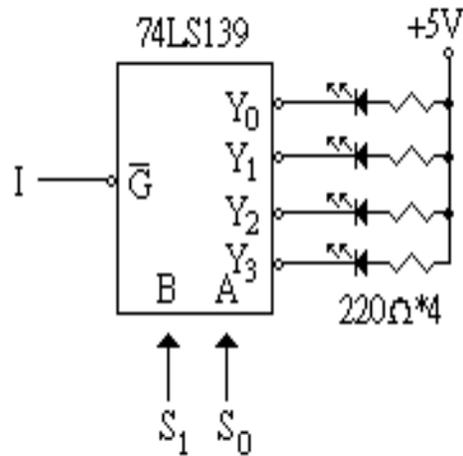


Figure 5-8 1 to 4 DUMX circuit

2. Input: Connect CON7 S1 to CON1 IN1  
 Connect CON7 S2 to CON1 IN2  
 Connect CON7 S3 to CON1 IN3
- Output: Connect CON4 OUT1 to LED DISPLAY CON15 Q9  
 Connect CON4 OUT2 to LED DISPLAY CON15 Q10  
 Connect CON4 OUT3 to LED DISPLAY CON15 Q11  
 Connect CON4 OUT4 to LED DISPLAY CON15 Q12
3. Record LED changes in table 5-3, when LED is on, Y=0, when LED is off, Y=1.

Input			Output			
I	S <sub>1</sub>	S <sub>0</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
0	0	0				
1	0	0				
0	0	1				
1	0	1				
0	1	0				
1	1	0				
0	1	1				
1	1	1				

Table 5-3 Truth table

4. From table 5-3, we know when S<sub>1</sub>S<sub>0</sub>=00, Y<sub>0</sub>Y<sub>1</sub>Y<sub>2</sub>Y<sub>3</sub>=\_\_\_\_, when S<sub>1</sub>S<sub>0</sub>=01, Y<sub>0</sub>Y<sub>1</sub>Y<sub>2</sub>Y<sub>3</sub>=\_\_\_\_ when S<sub>1</sub>S<sub>0</sub>=10, Y<sub>0</sub>Y<sub>1</sub>Y<sub>2</sub>Y<sub>3</sub>=\_\_\_\_, when S<sub>1</sub>S<sub>0</sub>=11, Y<sub>0</sub>Y<sub>1</sub>Y<sub>2</sub>Y<sub>3</sub>=\_\_\_\_.

#### 5-4 Questions and Discussion

1. What decides the input of MUX output?
2. Assume there is a 32 input lines MUX, then what is the logic input?
3. By using 8 of 1 data selector/MUX design to match the following logic function circuit.

$$\bar{E} = \bar{A} \cdot \bar{B} \cdot C \cdot D + A \cdot B \cdot \bar{C} + A \cdot B \cdot \bar{D}$$